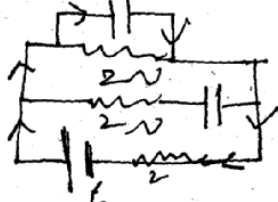
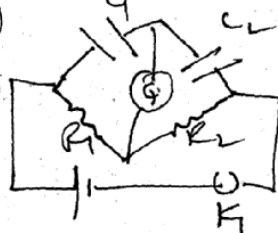
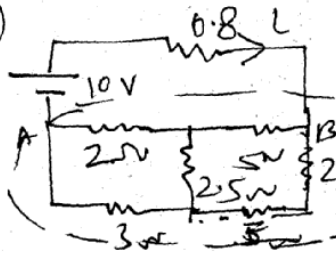


PHYSICS

Q.1. (a)  $i = \frac{6}{2} = 3 \text{ Amp}$ (1)

Q.2 (d)  for the balancing
 $\frac{C_1}{R_1} = \frac{C_2}{R_2}$
 $\frac{C}{5} = \frac{6}{2} \Rightarrow C = 15 \mu\text{f}$

Q.3. (a)  This is a balanced Wheatstone bridge
eq. R = 4.2


Total resistance of the circuit = 5Ω
The current through 8Ω = $\frac{10}{5} = 2 \text{ Amp}$
 $V_A + 10 - 2 \times 0.8 = V_B \Rightarrow V_A - V_B = -1.4 \text{ V}$.

Q.4. (c) As the potential energy of the system depends upon the relative orientation & position of the dipoles, it remains same. So work done = zero.

5. (a) Electric field due to $-r_0 \text{ part} = \frac{3}{4} \left(\frac{\sigma}{2\epsilon_0} \right)$
" " " $+r_0 \text{ part} = \frac{1}{4} \left(\frac{\sigma}{2\epsilon_0} \right)$
Net electric field downwards = $\frac{\sigma}{4\epsilon_0}$
The displacement is against the electric force
 $w = -\frac{\sigma}{4\epsilon_0} d$

(2)

6. (a)

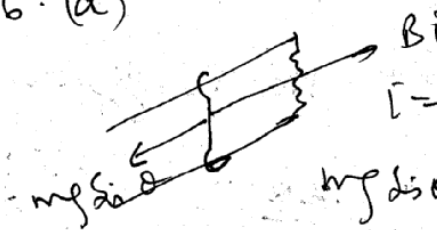

$i = \frac{Bvl}{R}$
 $mg \sin \theta = B \times \frac{Bvl}{R} \times l$
 $v = \frac{mgR \sin \theta}{B^2 l^2}$

7. (c) $\frac{200}{R} = 2 \Rightarrow R = 100$

Then $\frac{400}{\sqrt{(100)^2 + (20 \times 50 L)^2}} = 2 \Rightarrow L = 0.55 \text{ H}$

9. $F = B i R \sqrt{2}$ Hence $F' = B i \times 2R$
 So $F' = \frac{E}{\sqrt{2}} \times 2 = F \sqrt{2}$

8. (c) $\sqrt{2} = \frac{V_0}{Z}$ & $1 = \frac{V_0}{Z} \sin \omega t$

$\Rightarrow \sin \omega t = \frac{1}{\sqrt{2}}$ also $Z = \sqrt{(X_L - X_C)^2 + R^2} = 50 \sqrt{10}$

So $V_A - V_B = V_{\text{instantaneous}} = V_0 \sin \omega t = 2 \times 1 \times \frac{1}{\sqrt{2}} = 50 \sqrt{5} \text{ V}$

10. (a) $\frac{Q_1}{3R} + \frac{Q_2}{3R} + \frac{Q_3}{3R} = 0$ (Other options may also be correct)

as $\frac{Q_1}{R} + \frac{Q_2}{2R} + \frac{Q_3}{3R} = 0$ is also correct

11. (a) $V_p = V \Rightarrow V_q = 4V$

$\Rightarrow q(V_q - V_p) = \frac{1}{2} m v^2 = q \cdot 3V$

$\Rightarrow v = \sqrt{\frac{6qV}{m}}$


(3)

12. (b)

$$K \frac{B}{a} - K \frac{2Q}{1.2a} = K \frac{Q}{r} - K \frac{2Q}{r}$$

$$\Rightarrow r = 1.5a$$

13. (a)

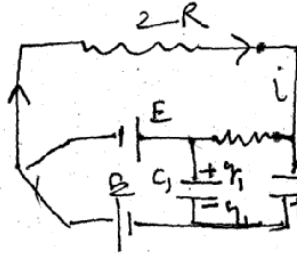

$$i = \frac{E}{3R}$$


Voltage across $C_1 = 2E$

Voltage across $C_2 = 2E \Rightarrow \frac{E}{3} = \frac{5E}{3}$

$$\text{So } \frac{1}{2} C_1 \times 4E^2 = \frac{1}{2} C_2 \times \frac{25}{9} E^2$$

$$C_1/C_2 = \frac{25}{36}$$

14. (b)

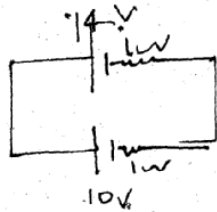

$$i = \frac{14-10}{2} = \frac{4}{2} = 2 \text{ Amp}$$


Power given to smaller

$$\text{cell} = 6i = 10 \times 2 = 20 \text{ W}$$

15. (a)

Electric field b/w the plates depends only upon the charge on the capacitor, which remains constant. So, the E. will remain constant.


16. (a)

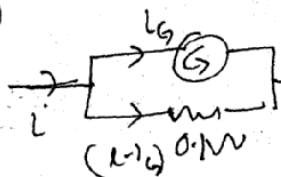

$$i_G = \frac{i \times 0.1}{R_G + 0.1}$$

$$\Rightarrow i = \frac{100 \times 10^6 \times (100.1)}{...}$$

17. (b)

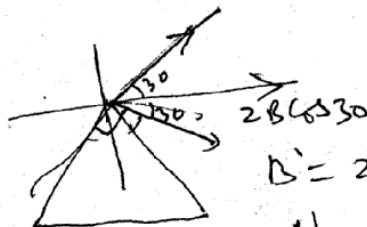

$$i = 10^{-3} \times 100.1$$


$$B' = 2 \frac{60}{20} \times \frac{L}{4 \times 10^2} \times \frac{\sqrt{3}}{2} = \frac{A \times 10^7 \times 2 \times \sqrt{3}}{4 \times 10^2}$$


$$B' = 10^5 \times \sqrt{3}$$


18. (a) After one revolution (Helical path) (4)

19. (b) $i = i_0 (1 - e^{-tR/L}) = \frac{V}{R} (1 - e^{-\frac{tR}{L}})$
 Distribution of current in $L \& 2L$ will be as the inverse ratio of the value of its distance

$$\left(\frac{1}{L} = \frac{1}{L} + \frac{1}{2L}\right)$$

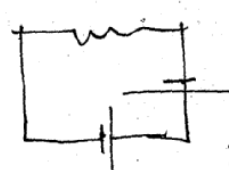
20. (a)  Induced EMF = $A \frac{d\phi}{dt} = 2.160V$
 $i = \frac{4.0 - 2.160}{10} = 0.18A$

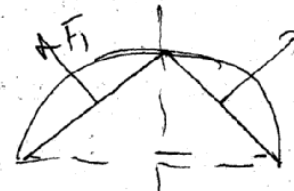21. (c) 
 $F_1 = B_0 i R \sqrt{2}$
 $F_2 = 2B_0 i R \sqrt{2}$
 $F = \sqrt{F_1^2 + F_2^2} = B_0 i R \sqrt{2+8} = B_0 i R \sqrt{10}$

22. (d) 
 Electric flux due to +q ($\frac{q}{2\epsilon_0}$, above) $\frac{q}{2\epsilon_0}$ (field downwards)
 Electric flux due to the charge -q at the corner $\frac{q}{24\epsilon_0}$ (field downwards)
 Total flux $\left(\frac{q}{2\epsilon_0} + \frac{q}{24\epsilon_0}\right)$

24 (b) $V_{ac} = V_{ab} + V_{bc}$
 $= Bv \cdot a + 0$

24 (c)

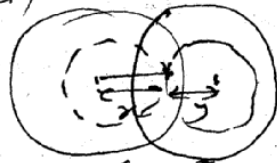

Net current flows in the superposed part -
 (By the superposition of the two current) net current will become zero.)

$B_1 \times 2\pi x = \mu_0 j \pi x^2$ & $B_2 \times 2\pi y = (\mu_0 j \pi y^2)$

$B_1 = \frac{\mu_0 j x}{2}$ & $B_2 = \left(-\frac{\mu_0 j}{2} y\right)$

$B = B_1 + B_2 = \frac{\mu_0 j}{2} (x+y) = \frac{\mu_0 j}{2} (d)$

25. (d) The path will be helical $t = \frac{2\pi}{B_0 \alpha} = \frac{T}{2}$

$x = \frac{v_0 \pi}{B_0 \alpha}$, as the half revolution will be completed $y=0$ & $z = -2R$ $\left[R = \frac{mv}{qB}\right]$

26. (d)

$M = \int \frac{q \times 2\pi x}{2\pi r^2} dx \cdot \frac{w}{2\pi} = \frac{qwr^2}{4}$


$\vec{J} = \vec{M} \times \vec{B} = \frac{qwr^2 B}{4} \hat{z}$ on the disc
 anticlockwise, so on the axis it will be clockwise.

27 .. (a)

$F = B il = B \frac{dq}{dt} l$

$\Delta p = F \Delta t = B dq l$

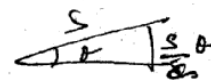$K_E = \frac{p^2}{2m} = \frac{B^2 (dq)^2 l^2}{2m} = \text{gain of p.e.} = m g \Delta s \sin \theta$
 calculate (dq)



28. (v) In the steady state current through the inductor $i = \left(\frac{E}{Y}\right)$

So energy stored across inductor.

$$U = \frac{1}{2} L \left(\frac{E}{Y}\right)^2$$

This ~~heat~~ energy will be generated in the form of heat across ~~R~~ R in the proportionality of the resistance.

So heat across $r = \frac{1}{2} L \left(\frac{E}{Y}\right)^2 \times \frac{r}{R+r}$

29. (c)

$$\frac{E}{6} = i \times \frac{5}{(5+R_6)} \Rightarrow 5+R_6 = 30$$

$$R_6 = 25$$

$$i \cdot R = \frac{5}{6}$$

So then

$$i' = i \times \frac{5}{(5+25)} = \frac{5}{5+150} = \frac{5}{155} i$$

$$i' = i \times \frac{1}{31}$$

30. (d)

$$i = \frac{(E - E_0)}{R + R_0}$$

$$V_a + E - iR = V_b$$

$$V_a - V_b = iR - E = \left(\frac{E - E_0}{R + R_0}\right)R - E$$

$$= V_c - V_d$$

$$V_c + E + \frac{q}{C} = V_d \quad \text{Keep the value of } V_c - V_d \text{ from above}$$

